

## HM 4

## 0. Around 25 hours

## Hazard unit Code

```

module hazunit(input[4:0] RsE, RtE, RsD,RtD, WriteRegM, WriteRegW, WriteRegE,
               input RegWriteE, RegWriteM, RegWriteW, MemtoRegE,MemtoRegM,
               BranchD, Jump,
               output [1:0] ForwardAE, ForwardBE,
               output StallF, StallD, FlushE, ForwardAD, ForwardBD);

reg lwstall, branchstall, superstall, jumpstall;
reg [1:0] ForwardAEReg, ForwardBEReg;
reg ForwardADReg, ForwardBDReg;

always @(*) begin //Forward AE and ForwardBE
    if ((RsE !=0) && (RsE == WriteRegM) && (RegWriteM))
        ForwardAEReg <= 10;
    else if ((RsE !=0) && (RsE == WriteRegW) && (RegWriteW))
        ForwardAEReg <= 01;
    else
        ForwardAEReg <= 00;

    if ((RtE !=0) && (RtE == WriteRegM) && (RegWriteM))
        ForwardBEReg <= 10;
    else if ((RtE !=0) && (RtE == WriteRegW) && (RegWriteW))
        ForwardBEReg <= 01;
    else
        ForwardBEReg <= 00;

    //Forward AD and Forward BD
    ForwardADReg <= (RsD !=0) && (RsD == WriteRegM) && RegWriteM;
    ForwardBDReg <= (RtD !=0) && (RtD == WriteRegM) && RegWriteM;

    //LWstall
    lwstall <= ((RsD == RtE) || (RtD == RtE)) && MemtoRegE;

    //Branch Stall
    branchstall <= (BranchD && RegWriteE && (WriteRegE == RsD ||
WriteRegE == RtD)) ||
                   (BranchD && MemtoRegM && (WriteRegM == RsD ||
WriteRegM == RtD));
    //Jump Stall
    jumpstall <= (Jump && RegWriteE && (WriteRegE == RsD || WriteRegE ==
RtD)) ||
                 (Jump && MemtoRegM && (WriteRegM == RsD || WriteRegM ==
RtD));

    superstall <= lwstall || branchstall || jumpstall;

```

```

    end
    //Assigning Outputs
    assign ForwardAE = ForwardAEReg;
    assign ForwardBE = ForwardBEReg;

    assign ForwardAD = ForwardADReg;
    assign ForwardBD = ForwardBDReg;

    assign StallF = superstall;
    assign StallD = superstall;
    assign FlushE = superstall;

endmodule

```

## Hazard Unit Testbench

```

module testbenchhaz();
    reg        clk, reset;
    reg[4:0]    RsE, RtE, RsD, RtD, WriteRegM, WriteRegW, WriteRegE;
    reg        RegWriteE, RegWriteM, RegWriteW, MemtoRegE, MemtoRegM, BranchD;
    wire[1:0]   ForwardAE, ForwardBE;
    wire        StallF, StallD, FlushE, ForwardAD, ForwardBD;

    // instantiate device under test
    hazunit dut(RsE, RtE, RsD, RtD, WriteRegM, WriteRegW, WriteRegE,
                RegWriteE, RegWriteM, RegWriteW, MemtoRegE, MemtoRegM,
BranchD,
                ForwardAE, ForwardBE,
                StallF, StallD, FlushE, ForwardAD, ForwardBD);

    initial begin
        $display("Test all zeros"); #10;
        RsE = 0; RtE = 0; RsD = 0; RtD = 0; WriteRegM = 0; WriteRegW = 0;
        WriteRegE = 0; RegWriteE = 0; MemtoRegE = 0; MemtoRegM = 0; RegWriteM =
0; RegWriteW = 0; BranchD = 0; #10
        $display("ForwardAD = %b, ForwardBD = %b, StallD = %b, StallF = %b,
FlushE = %b, ForwardAE = %b, ForwardBE = %b",
        ForwardAD, ForwardBD, StallD, StallF, FlushE, ForwardAE, ForwardBE); #10;

        $display("Testing RsE Mem Data"); #10;
        RsE = 1; RtE = 2; RsD = 3; RtD = 4; WriteRegM = 1; WriteRegW = 5;
        WriteRegE = 6; RegWriteE = 0; RegWriteM = 1; RegWriteW = 0; BranchD = 0;
#10
        $display("ForwardAD = %b, ForwardBD = %b, StallD = %b, StallF = %b,
FlushE = %b, ForwardAE = %b, ForwardBE = %b Expected ForwardAE = 10",
        ForwardAD, ForwardBD, StallD, StallF, FlushE, ForwardAE, ForwardBE); #10;

        $display("Testing RsE Write Back Data "); #10;
        RsE = 1; RtE = 2; RsD = 3; RtD = 4; WriteRegM = 8; WriteRegW = 1;
        WriteRegE = 6; RegWriteE = 0; RegWriteM = 1; RegWriteW = 1; BranchD = 0;
#10
    end
endmodule

```

```

    $display("ForwardAD = %b, ForwardBD = %b, StallD = %b, StallF = %b,
FlushE = %b, ForwardAE = %b, ForwardBE = %b Expected ForwardAE = 01",
    ForwardAD, ForwardBD, StallD, StallF, FlushE, ForwardAE, ForwardBE); #10;

    $display("Testing RsE with no Data Hazards "); #10;
    RsE = 1; RtE = 2; RsD = 3; RtD = 4; WriteRegM = 8; WriteRegW = 5;
    WriteRegE = 6; RegWriteE = 0; RegWriteM = 1; RegWriteW = 1; BranchD = 0;
#10
    $display("ForwardAD = %b, ForwardBD = %b, StallD = %b, StallF = %b,
FlushE = %b, ForwardAE = %b, ForwardBE = %b Expected ForwardAE = 00",
    ForwardAD, ForwardBD, StallD, StallF, FlushE, ForwardAE, ForwardBE); #10;

    $display("Testing RtE Mem Back Data Hazard"); #10;
    RsE = 1; RtE = 2; RsD = 3; RtD = 4; WriteRegM = 2; WriteRegW = 5;
    WriteRegE = 6; RegWriteE = 0; RegWriteM = 1; RegWriteW = 1; BranchD = 0;
#10
    $display("ForwardAD = %b, ForwardBD = %b, StallD = %b, StallF = %b,
FlushE = %b, ForwardAE = %b, ForwardBE = %b Expected ForwardBE = 10",
    ForwardAD, ForwardBD, StallD, StallF, FlushE, ForwardAE, ForwardBE); #10;

    $display("Testing RtE Write Back Data Hazard"); #10;
    RsE = 1; RtE = 2; RsD = 3; RtD = 4; WriteRegM = 8; WriteRegW = 2;
    WriteRegE = 6; RegWriteE = 0; RegWriteM = 1; RegWriteW = 1; BranchD = 0;
#10
    $display("ForwardAD = %b, ForwardBD = %b, StallD = %b, StallF = %b,
FlushE = %b, ForwardAE = %b, ForwardBE = %b Expected ForwardBE = 01",
    ForwardAD, ForwardBD, StallD, StallF, FlushE, ForwardAE, ForwardBE); #10;

    $display("Testing RsE No Data Hazard "); #10;
    RsE = 1; RtE = 2; RsD = 3; RtD = 4; WriteRegM = 8; WriteRegW = 5;
    WriteRegE = 6; RegWriteE = 0; RegWriteM = 1; RegWriteW = 1; BranchD = 0;
#10
    $display("ForwardAD = %b, ForwardBD = %b, StallD = %b, StallF = %b,
FlushE = %b, ForwardAE = %b, ForwardBE = %b Expected ForwardBE = 00",
    ForwardAD, ForwardBD, StallD, StallF, FlushE, ForwardAE, ForwardBE); #10;

    $display("Testing LW Stall/ RsD == RtE"); #10;
    RsE = 1; RtE = 2; RsD = 2; RtD = 4; WriteRegM = 8; WriteRegW = 5;
    WriteRegE = 6; RegWriteE = 0; RegWriteM = 1; RegWriteW = 1; MemtoRegE =
1; MemtoRegM = 0; BranchD = 0; #10
    $display("ForwardAD = %b, ForwardBD = %b, StallD = %b, StallF = %b,
FlushE = %b, ForwardAE = %b, ForwardBE = %b Expected Flush = 1",
    ForwardAD, ForwardBD, StallD, StallF, FlushE, ForwardAE, ForwardBE); #10;

    $display("Testing LW Stall/ RtD == RtE"); #10;
    RsE = 1; RtE = 2; RsD = 3; RtD = 2; WriteRegM = 8; WriteRegW = 5;
    WriteRegE = 6; RegWriteE = 0; RegWriteM = 1; RegWriteW = 1; MemtoRegE =
1; MemtoRegM = 0; BranchD = 0; #10
    $display("ForwardAD = %b, ForwardBD = %b, StallD = %b, StallF = %b,
FlushE = %b, ForwardAE = %b, ForwardBE = %b Expected Flush = 1",
    ForwardAD, ForwardBD, StallD, StallF, FlushE, ForwardAE, ForwardBE); #10;

    $display("Testing ForwardAD"); #10;
    RsE = 1; RtE = 2; RsD = 2; RtD = 4; WriteRegM = 2; WriteRegW = 5;
    WriteRegE = 6; RegWriteE = 0; RegWriteM = 1; RegWriteW = 1; MemtoRegE =
1; MemtoRegM = 0; BranchD = 0; #10

```

```

    $display("ForwardAD = %b, ForwardBD = %b, StallD = %b, StallF = %b,
FlushE = %b, ForwardAE = %b, ForwardBE = %b Expected ForwardAD = 1",
    ForwardAD, ForwardBD, StallD, StallF, FlushE, ForwardAE, ForwardBE); #10;

    $display("Testing ForwardBD"); #10;
    RsE = 1; RtE = 2; RsD = 2; RtD = 4; WriteRegM = 4; WriteRegW = 5;
    WriteRegE = 6; RegWriteE = 0; RegWriteM = 1; RegWriteW = 1; MemtoRegE =
1; MemtoRegM = 0; BranchD = 0; #10
    $display("ForwardAD = %b, ForwardBD = %b, StallD = %b, StallF = %b,
FlushE = %b, ForwardAE = %b, ForwardBE = %b Expected ForwardBD = 1",
    ForwardAD, ForwardBD, StallD, StallF, FlushE, ForwardAE, ForwardBE); #10;

    $display("Testing Branch Stall Execute Stage"); #10;
    RsE = 1; RtE = 2; RsD = 3; RtD = 4; WriteRegM = 8; WriteRegW = 5;
    WriteRegE = 3; RegWriteE = 1; RegWriteM = 1; RegWriteW = 1; MemtoRegE =
1; MemtoRegM = 0; BranchD = 1; #10
    $display("ForwardAD = %b, ForwardBD = %b, StallD = %b, StallF = %b,
FlushE = %b, ForwardAE = %b, ForwardBE = %b Expected Flush = 1",
    ForwardAD, ForwardBD, StallD, StallF, FlushE, ForwardAE, ForwardBE); #10;

    $display("Testing Branch Memory Stage"); #10;
    RsE = 1; RtE = 2; RsD = 6; RtD = 4; WriteRegM = 6; WriteRegW = 5;
    WriteRegE = 10; RegWriteE = 0; RegWriteM = 1; RegWriteW = 1; MemtoRegE =
1; MemtoRegM = 1; BranchD = 1; #10
    $display("ForwardAD = %b, ForwardBD = %b, StallD = %b, StallF = %b,
FlushE = %b, ForwardAE = %b, ForwardBE = %b Expected Flush = 1",
    ForwardAD, ForwardBD, StallD, StallF, FlushE, ForwardAE, ForwardBE); #10;

end
endmodule

```

There is no test vectors because I just tested the cases without a reading in a file.

## Hazard Unit Waveform

Below is the waveform generated from the test bench.

+	RS0	00000	00000	00011																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																
---	-----	-------	-------	-------	--	--	--	--	--

[illegible]

## Pipelined Processor Code

```
//-----
// mipssingle.v
// Sarah_Harris@hmc.edu 22 June 2007
// Single-cycle MIPS processor
//-----

// multi-cycle MIPS processor

module controller(input  [5:0] op, funct,
                  input    zero,
                  output    memtoreg, memwrite,
                  output    alusrc,      // LUI
                  output    regdst,      // JAL
                  output    regwrite,
                  output    Jump,
                  output [3:0] alucontrol, // 4 bits for SLL
                  input    ltez,        // BLEZ
                  output    jal,         // JAL
                  output    BranchD);    // BranchD

wire [1:0] aluop;
wire    branch;
wire    blez; // BLEZ and JAL not Used, they wires do connect
            //any where in the datapath.

maindec md(op, memtoreg, memwrite, branch,
           alusrc, regdst, regwrite, Jump,
           aluop, blez, jal, BranchD); // BLEZ, JAL, BranchD
aludec ad(funct, aluop, alucontrol);

endmodule

//Maindecoder
//Alu src and regdst have been reduced to one bit
//since JAL and LUI are not used
module maindec(input  [5:0] op,
               output    memtoreg, memwrite,
               output    branch,
               output    alusrc, //
               output    regdst, // JAL
               output    regwrite,
               output    Jump,
               output [1:0] aluop,
               output    blez,    // BLEZ
               output    jal,     // JAL
               output    BranchD); // BranchD

reg [11:0] controls;
assign {regwrite, regdst, alusrc,
       branch, memwrite,
       memtoreg, Jump, aluop,
       blez,    // BLEZ
       jal,     // JAL
       BranchD} // BranchD
       = controls;
```

```

always @(*)
    case(op)
        6'b000000: controls <= 12'b1_1_0_0_0_0_0_10_0_0_0_0; //Rtype
        6'b100011: controls <= 12'b1_0_1_0_0_0_0_00_0_0_0_0; //LW
        6'b101011: controls <= 12'b0_0_1_0_1_0_0_00_0_0_0_0; //SW
        6'b000100: controls <= 12'b0_0_0_0_0_1_0_00_0_1_1_1; //BEQ
        6'b001000: controls <= 12'b1_0_1_0_0_0_0_00_0_0_0_0; //ADDI
        6'b000010: controls <= 12'b0_0_0_0_0_0_0_1_00_0_0_0; //J
        //6'b001010: controls <= 12'b1_0_001000011000; //SLTI
        //6'b001111: controls <= 14'b1001000000000000; //LUI
        //6'b000110: controls <= 14'b000000000001100; //BLEZ
        //6'b000011: controls <= 14'b11000000100010; //JAL
        //6'b100001: controls <= 14'b10001001000001; // LH
        default: controls <= 12'bxxxxxxxxxxx; //???
    endcase
endmodule

module aludec(input [5:0] funct,
              input [1:0] aluop,
              output reg [3:0] alucontrol); // 4-bits for SLL

always @(*)
    case(aluop)
        2'b00: alucontrol <= 4'b0010; // add
        2'b01: alucontrol <= 4'b1010; // sub
        2'b11: alucontrol <= 4'b1011; // slt
        default: case(funct) // RTYPE
            6'b100000: alucontrol <= 4'b0010; // ADD
            6'b100010: alucontrol <= 4'b1010; // SUB
            6'b100100: alucontrol <= 4'b0000; // AND
            6'b100101: alucontrol <= 4'b0001; // OR
            6'b101010: alucontrol <= 4'b1011; // SLT
            //6'b000000: alucontrol <= 4'b0100; // SLL
            default: alucontrol <= 4'bxxxx; // ???
        endcase
    endcase
endmodule

module datapath(input clk, reset,
               output [31:0] pcF,
               output [31:0] ReadDataW, WriteDataM, ResultsW,
               output MemWriteM
               );

//Wires Next PC Logic
wire [31:0] pcnext, pcnextbr, pcplus4, pcbranch;
wire [31:0] InstrF;

//Not inputted Anywhere Only used for as Place Keeper in ALU
wire zero;

//Wire Fetch Register
wire [31:0] pcplus4F;

```



```

//Wires for Decode Register
    wire [31:0] InstrD, pcplus4D, pcBranchD, signImmD, RD1BMuxD, RD2BMuxD,
RD1AMuxD, RD2AMuxD;
    wire [31:0] signImmshD;
    wire [3:0] AluControlD;
    wire equalD, PCSrcD, RegWriteD, MemtoRegD, MemWriteD, AluSrcD, RegDstD,
BranchD;

    //Wires for Execute
    wire[31:0] RD1AMuxE, RD2AMuxE, AluOutE, SrcAE, SrcBE, WriteDataE,
signImmE;
    wire[4:0] RsE, RtE, RdE, WriteRegE, ShamtE;
    wire[3:0] AluControlE;
    wire RegWriteE, MemtoRegE, MemWriteE, AluSrcE, RegDstE;

    //Wire for Memory
    wire[31:0] AluOutM, ReadDataM;
    wire[4:0] WriteRegM;
    wire RegWriteM, MemtoRegM;

    //Wire For Write Back
    wire[31:0] AluOutW;
    wire[4:0] WriteRegW;
    wire RegWriteW, MemtoRegW;

    //Haz unit wires
    wire[1:0] ForwardAE, ForwardBE;
    wire StallD, StallF, FlushE, ForwardAD, ForwardBD;

    //Hazard Unit
    hazunit hazunit(RsE, RtE, InstrD[25:21], InstrD[20:16], WriteRegM,
WriteRegW, WriteRegE,
                    RegWriteE, RegWriteM, RegWriteW, MemtoRegE, MemtoRegM,
BranchD, Jump,
                    ForwardAE, ForwardBE,
                    StallF, StallD, FlushE, ForwardAD, ForwardBD);

    //Controller
    controller c(InstrD[31:26], InstrD[5:0], zero,
                MemtoRegD, MemWriteD,
                AluSrcD, RegDstD, RegWriteD, Jump,
                AluControlD,
                ltez, // BLEZ
                jal, // JAL
                BranchD); // BranchD

    //Instruction and Data Memory
    imem imem(pcF[7:2], InstrF);
    dmem dmem(clk, MemWriteM, AluOutM, WriteDataM,
                ReadDataM);

    //next PC Logic
    flopenr #(32) pcreg(clk, reset, StallF, pcnext, pcF);
    adder
    pcaddl(pcF, 32'b100, pcplus4F);

```

```

//Branch
sl2          immsh(signImmD, signImmshD);
adder        pcadd2(pcplus4D, signImmshD, pcBranchD);
mux2 #(32)   pcbrmux(pcplus4F, pcBranchD, PCSrcD, pcnextbr);
//Jump
mux2 #(32)   pcmux(pcnextbr, {pcplus4D[31:28], InstrD[25:0], 2'b00},
Jump, pcnext);

//RegisterFile
regfile      rf(clk, RegWriteW, InstrD[25:21], InstrD[20:16],
WriteRegW, ResultsW,
             RD1BMuxD, RD2BMuxD);

//Branch and Jump Data Hazard Mux
mux2 #(32)    br1mux(RD1BMuxD, AluOutM, ForwardAD, RD1AMuxD);
mux2 #(32)    br2mux(RD2BMuxD, AluOutM, ForwardBD, RD2AMuxD);
equalReg      eq(RD1AMuxD, RD2AMuxD, equalD);
and2          BAnd(BranchD, equalD, PCSrcD);

//WriteRegE Mux
mux2 #(5)     wrmux(RtE, RdE, RegDstE, WriteRegE);

//ForwardAE Mux
mux3 #(32)    faemux(RD1AMuxE, ResultsW, AluOutM, ForwardAE, SrcAE);

//ForwardBE Mux
mux3 #(32)    fbemux(RD2AMuxE, ResultsW, AluOutM, ForwardBE,
WriteDataE);

//Immediate or Register Mux
mux2 #(32)    immux(WriteDataE, signImmE, AluSrcE, SrcBE);

//ALU
alu           alu(SrcAE, SrcBE, AluControlE, ShamTE,
                AluOutE, zero, ltez); //last two bits not used

//Data Memory output Mux
mux2 #(32)    memmux(AluOutW, ReadDataW, MemtoRegW, ResultsW);

//signExt
signext       se(InstrD[15:0], signImmD);

//Fetch Register
floprrFet     floprrFet(clk, reset | PCSrcD | Jump, StallD, PCSrcD,
pcplus4F, InstrF,
                pcplus4D, InstrD);

//Decode Register
floprrDec     floprrDec(clk, reset | FlushE, FlushE, RD1AMuxD, RD2AMuxD,
signImmD,
                InstrD[25:21], InstrD[20:16], InstrD[15:11],
InstrD[10:6],

```

```

RegWriteD, MemtoRegD, MemWriteD, AluSrcD,
RegDstD,
signImmE,
BranchD, AluControlD, RD1AMuxE, RD2AMuxE,
RsE, RtE, RdE, ShamtE, RegWriteE, MemtoRegE,
MemWriteE,
AluSrcE, RegDstE, AluControlE);


//Execute Register
flopExe flopExe(clk, reset, AluOutE, WriteDataE, WriteRegE,
RegWriteE,
MemtoRegE, MemWriteE, AluOutM, WriteDataM,
WriteRegM,
RegWriteM, MemtoRegM, MemWriteM);


//Memory Register
flopMem flopMem(clk, reset, AluOutM, ReadDataM, WriteRegM,
RegWriteM,
MemtoRegM, AluOutW, ReadDataW, WriteRegW,
RegWriteW,
MemtoRegW);

endmodule

```

[illegible]

 

 

In the first waveform picture, after the reset, and on PC 4, the register file gets instruction 2002005. It is addi \$2, \$0, 5. The results will be written after 4 cycles and is seen in the ResultsW signal. The next instruction is 2003000c, addi \$3, \$0, 12. It won't be written into the Register File until after 4 cycles. The next instruction 2067fff7, addi \$7, \$3, -9. This is an instance of having forward the ALU result from the Memory stage to the Execute stage because of \$3 hasn't been written. It does get the right value because of 4 cycles, 3 is written into the Register File. The next instruction is 00e22025, or \$4, \$7, \$2. It is another case of forwarding from the Memory to the Execute stage with \$7 being the hazard. The correct is written as shown in the second waveform picture. The next two instructions are ANDs with the second instruction being forwarded data from the Memory stage because \$5.

At the start of the second waveform picture, the first beq instruction is decoded. Due to the Data hazard of \$5 being written in yet, the instruction is stalled to pass it in. That is why this instruction takes two clock cycles as shown in the waveform. It doesn't take the branch as it should. It falls through because the next instruction is 0064202a, slt \$4, \$3, \$4. The next instruction is the next beq instruction. Once again, it the instruction is stalled for \$4 from the previous cycle to be calculated. This time it should take the branch. At this point it, stalls and allows the instruction to pass through. Instruction 00e2202a, slt \$4, \$7, \$2. The next instruction, 0085320, goes through no problem.

At the start of the third waveform picture, the next instruction 00e23822, sub \$7, \$7, \$2, does have a data hazard. \$7 must be forwarded from memory. The value in \$7 can be seen in ReadDataM. The next instruction ac670044, sw \$7, 68(\$3), needs get the value of \$7 forwarded from memory. The next instruction is 8c020050, lw \$2, 80(\$0). No stall is need for this instruction. The next instruction is 08000011, j end. It is taken immediately, and the next instruction is cleared. After one cycle, the next instruction, ac020054, is passed in. ac020054, sw \$2, 84(\$0), saves the right value in memory.